

## Practise Problems-I

- For the circuit in the below figure 1,  $i_s = 30\cos 10^5 t$  A. Find the average power absorbed by the  $50\Omega$  resistor.

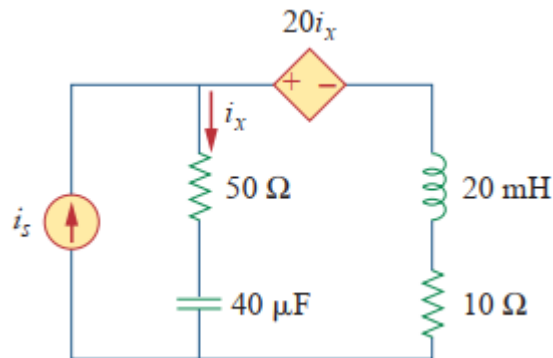


Figure 1

- For the circuit in the below figure 2, Find the average power absorbed by the  $10\Omega$  resistor.

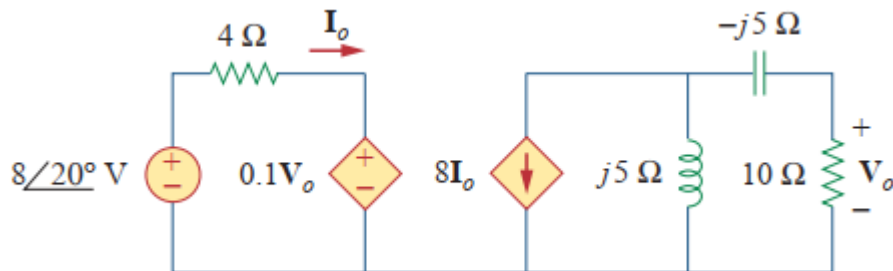


Figure 2

- Assume the value of  $v_s = 16 \cos (2t - 40^\circ)$  V in the below circuit i.e. figure 3, find the average power delivered to each of the passive elements.

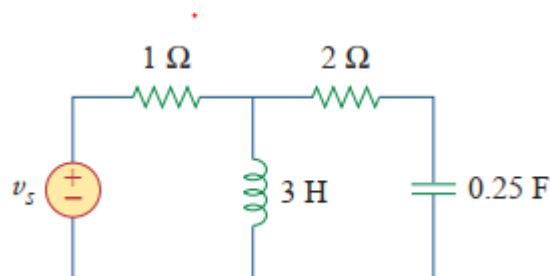


Figure 3

4. Find the value of  $Z_L$  in the below figure 4 for maximum power transfer.

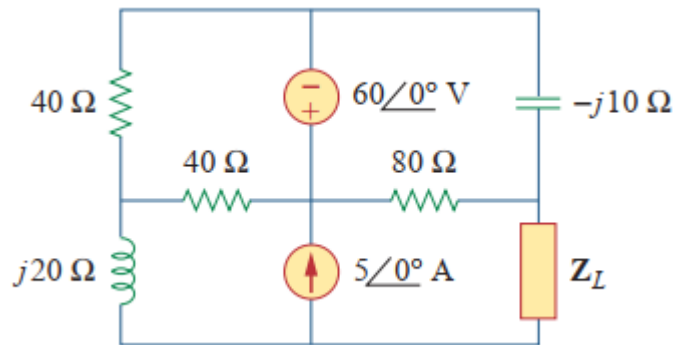


Figure 4

5. Assuming that the load impedance is to be purely resistive, what load should be connected to terminals  $a$ - $b$  of the circuits in figure 5 so that the maximum power is transferred to the load.

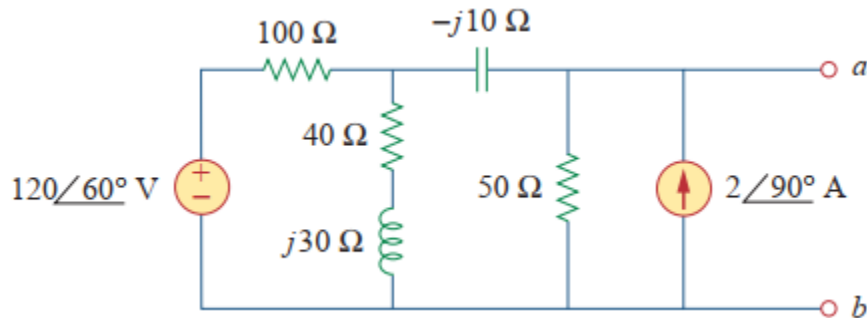


Figure 5

6. Find the complex power delivered by to the network in figure 6. Let  $v_s = 160\cos(2000t)$  V.

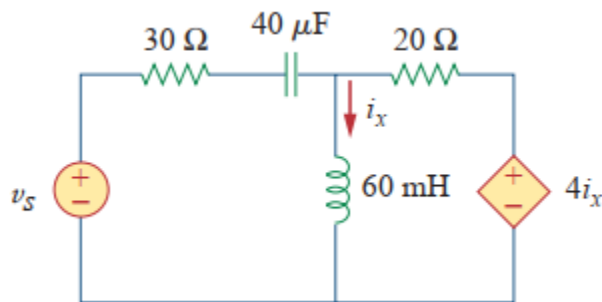


Figure 6

7. For the entire circuit in below figure 7. Calculate

- (a) Power factor
- (b) Average power delivered by the source.
- (c) Reactive power
- (d) Apparent power
- (e) Complex power

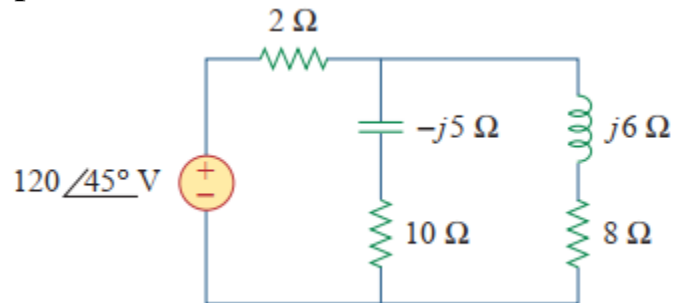


Figure 7

8. Obtain the complex power delivered to the  $10\text{k}\Omega$  resistor which is shown below in figure 8

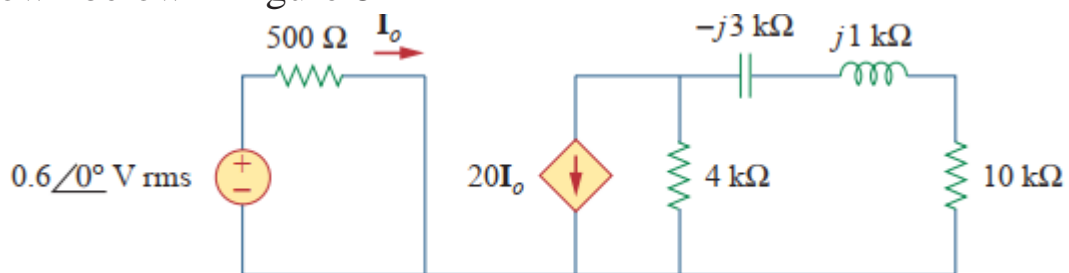


Figure 8

9. Calculate the reactive power in the inductor and capacitor in the circuit of Figure 9.

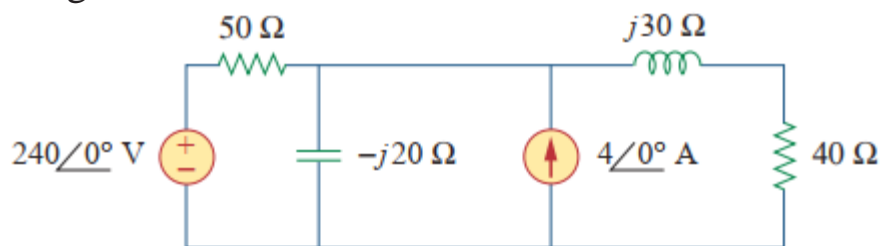


Figure 9