



---

# ECE380 Digital Logic

Implementation Technology:  
Look-up Tables, XOR and XNOR  
gates




## Look-up tables

---

- A logic block commonly used in FPGA devices is the ***look-up table*** (LUT)
- An LUT contains ***storage cells*** that are used to implement small logic functions
- Each cell is capable of storing a single logic value (0 or 1)
- Multiplexers are used to select one of the storage cells for output
- Essentially, the cells store the truth table for a function and the multiplexers select a particular cell for output based on a set of select (control) inputs



## Two-input LUT structure

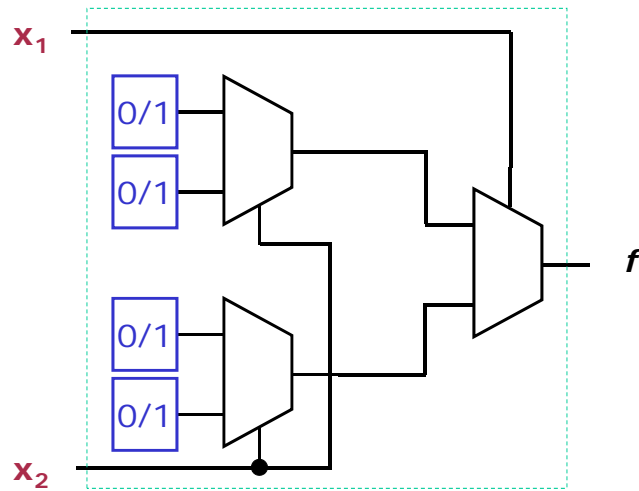


Electrical & Computer Engineering

Dr. D. J. Jackson Lecture 11-3


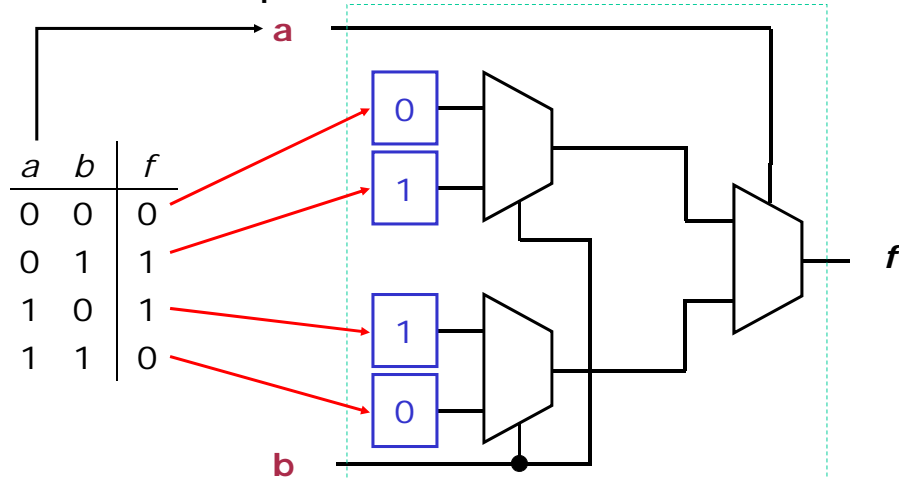
## Programmed LUT ( $f = a'b + ab'$ )

most significant variable  
controls last multiplexer




Electrical & Computer Engineering

Dr. D. J. Jackson Lecture 11-4



## Three-input LUT structure

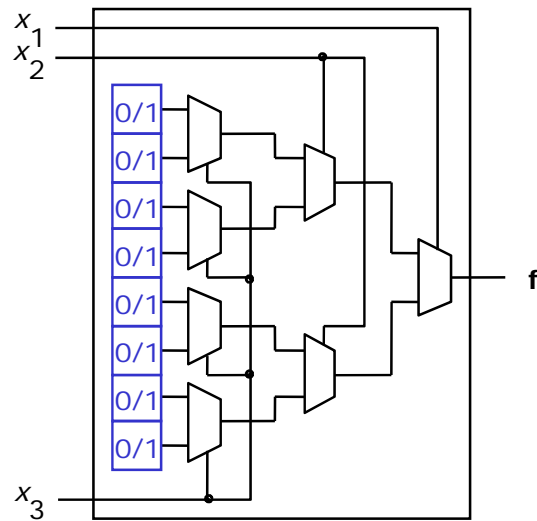

Electrical & Computer Engineering

Dr. D. J. Jackson Lecture 11-5



## Three-input LUT example

- Show the diagram for a programmed LUT that implements the function
- $f(a,b,c) = a'bc + abc' + ac$

Electrical & Computer Engineering


Dr. D. J. Jackson Lecture 11-6



## Exclusive OR (XOR) gate


- Another basic element, very useful in building circuits that perform arithmetic operations, is the exclusive OR (XOR) gate
- XOR function is denoted with the  $\oplus$  symbol
- In SOP form,  $a \oplus b = ab' + a'b$
- Output is '1' only if the inputs are different

| $a$ | $b$ | $a \oplus b$ |
|-----|-----|--------------|
| 0   | 0   | 0            |
| 0   | 1   | 1            |
| 1   | 0   | 1            |
| 1   | 1   | 0            |

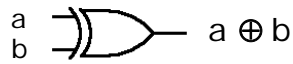
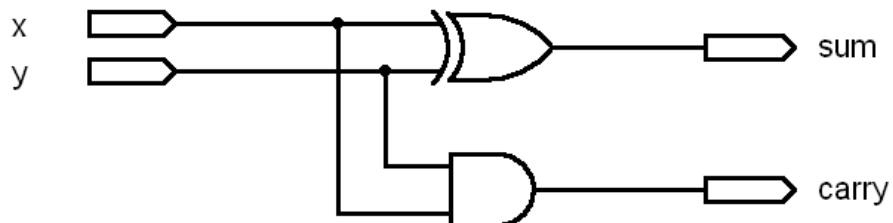
## Example XOR usage

- Recall the adder circuit
  - $\text{sum} = xy' + x'y$
  - $\text{carry} = xy$





## XOR of three variables

- What is the canonical SOP form for the following expression?


$$f(a,b,c) = a \oplus b \oplus c$$



## Exclusive NOR (XNOR) gate

- Derived from the XOR function, XNOR is the complement of XOR
- XNOR function is denoted with the  $\equiv$  symbol
- In SOP form,  $a \equiv b = (a \oplus b)' = ab + a'b'$
- Output is '1' only if the inputs are the same
- Also called an equivalence function

| <i>a</i> | <i>b</i> | $a \equiv b$ |
|----------|----------|--------------|
| 0        | 0        | 1            |
| 0        | 1        | 0            |
| 1        | 0        | 0            |
| 1        | 1        | 1            |

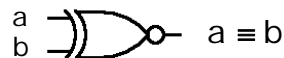



## XNOR of three variables

---

- What is the canonical SOP form for the following expression?

$$f(a,b,c) = a \equiv b \equiv c$$