

Applied Digital Logic Design

BOOLEAN LAWS

T1 : Commutative Law

(a) $A + B = B + A$

(b) $A B = B A$

T2 : Associative Law

(a) $(A + B) + C = A + (B + C)$

(b) $(A B) C = A (B C)$

T3 : Distributive Law

(a) $A (B + C) = A B + A C$

(b) $A + (B C) = (A + B) (A + C)$

T4 : Identity Law

(a) $A + A = A$

(b) $A A = A$

T5 : Negation Law

(a) $(\overline{\overline{A}}) = \overline{A}$

(b) $(\overline{\overline{\overline{A}}}) = A$

T6 : Redundancy Law

(a) $A + A B = A$

(b) $A (A + B) = A$

T7 :

(a) $0 + A = A$

(b) $1 A = A$

(c) $1 + A = 1$

(d) $0 A = 0$

T8 :

(a) $\overline{A} + A = 1$

(b) $\overline{A} A = 0$

T9 :

(a) $A + \overline{A} B = A + B$

(b) $A (\overline{A} + B) = A B$

T10 : De Morgan's Theorem

(a) $(\overline{A + B}) = \overline{A} \overline{B}$

(b) $(\overline{A B}) = \overline{A} + \overline{B}$

UNIVERSIAL LOGIC GATES : SIGNOFICNCE

Normal	Universal	Additional
NOT	NAND	XOR
AND	NOR	XNOR
OR		

❑ **NOT : 2 transistors (PMOS top and NMOS bottom)**
(R-C circuit) at Input "0": PMOS ON, charge "C" i.e. output to "1", at Input "1": NMOS ON, discharge "C" i.e. output to "0",

❑ **Input-output transfer characteristics**
 Output delay with input: speed limitation

❑ **OR : realization with NAND or NOR**

Area: NOR < NAND

Dynamic Power: NOR < NAND

Delay (Speed): NAND > NOR

TARGET:

- **Area & Power Minimization**
- **Speed Maximization**
- **Logic optimization (No of gate minimization)**

- NOT/AND /OR : realization with NAND or NOR : Universal
- NOT, NAND and NOR: CMOS realization with help of **De Morgan's Theorem**
- Example : $\text{NAND}(\overrightarrow{A.B}) \sim \overrightarrow{A} + \overrightarrow{B} : 4 \text{ transistors}$

NMOS section (Bottom) = $A.B$

PMOS section (Top) = $\overrightarrow{A} + \overrightarrow{B}$

$\text{NOR}(\overrightarrow{A + B}) \sim \overrightarrow{A} . \overrightarrow{B} : 4 \text{ transistors}$

NMOS section (Bottom) = $A+B$

PMOS section (Top) = $\overrightarrow{A} . \overrightarrow{B}$

OR and AND: 6 transistors , 4 nos NOR/NAND and 2 nos NOT

- NAND & NOR: CMOS (PMOS mobility < NMOS Mobilty)

Area: Same




Dynamic Power: NOR < NAND

Delay (Speed): NAND > NOR




Function : Optimization and logic realization

$$Y = \overline{(A + \bar{B})(\bar{B} + C)}$$

$$= A + C$$

  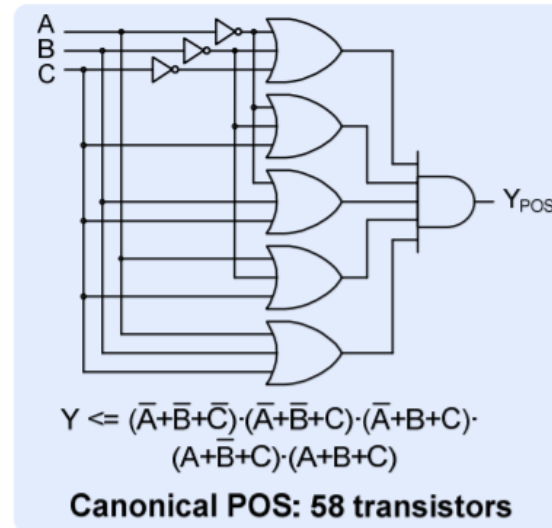

A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

  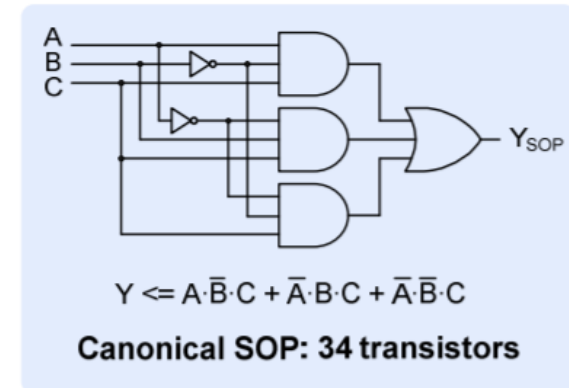

AND and Then OR (SOP), with "1"
 OR and Then AND (POS) with "0"

K-maps rule

- ❑ Minimize Boolean expressions of 3, 4 variables very easily using K-map without using any Boolean algebra theorems.
- ❑ K-map can take two forms Sum of Product (SOP) and Product of Sum (POS) according to the need of problem.
- ❑ K-map is table like representation but it gives more information than TRUTH TABLE. We fill grid of K-map with 0's and 1's then solve it by making groups.
- **Steps to solve expression using K-map-**
- Select K-map according to the number of variables.
- Identify minterms or maxterms as given in problem.
- For SOP put 1's in blocks of K-map respective to the minterms (0's elsewhere).
- For POS put 0's in blocks of K-map respective to the maxterms (1's elsewhere).
- Make rectangular groups containing total terms in power of two like 2,4,8 ..(except 1) and try to cover as many elements as you can in one group.
- From the groups made in step 5 find the product terms and sum them up for SOP form.

K-maps rule

❑ Few Link:

<http://www.ee.surrey.ac.uk/Projects/Labview/minimisation/karrules.html>

❑ http://www.ee.ic.ac.uk/pcheung/teaching/ee1_digital/Lecture5-Karnaugh%20Map.pdf

❑ <https://www.seas.upenn.edu/~cit595/cit595s10/lectures/kmap.pdf>

❑ <http://www.pitt.edu/~kmram/0132/lectures/karnaugh-maps.pdf>

❑ Tutorial with solved question: TA send soon

TA: List

		Phone	Area	Assign TA/Students (As per SI no. - please refer the student list)	
1	RASHI DUTT	ee16resch11014@iith.ac.in	879001 9514	VLSI	1-37
2	LISA SARKAR	EE16RESCH11011@iith.ac.in	910028 3763	VLSI	38-74
3	Uma Maheswari G	EE19MTECH01009@iith.ac.in	997056 6593	PEPS	1-24
4	Venkatesh Vayyavuru	ee19mtech01010@iith.ac.in	829782 1983	CSP	25-48
5					49-74
6	INDRANIL BHATTACHARJEE	ee16resch11009@iith.ac.in	918275 5954	VLSI	75-111
7	DINESH GUPTA	EE16RESCH11007@iith.ac.in	779987 7407	VLSI	111-147
8	Ruchir	EE19MTECH01006@iith.ac.in	991974 9222	VLSI	75-98
9	Vyshnavi Vangari	ee19mtech11024@iith.ac.in	833092 3207	CSP	99--122
10					123-147