

ID1330 : Applied Digital Logic Design Experiment


1. Design a clock divider circuit which provides input to a shift register and display the output on the oscilloscope.
2. Design a 4 bit adder circuit which takes inputs from the shift register and displays the output on a 7 segment display.
3. Design a complete system integrating the clock divider circuit along with the adder circuit and display the output on a 7 segment display.

List of equipments


1. IC 7400 – 2 input NAND Gate
2. IC 7486 – 2 input XOR Gate
3. IC 7447 – Decoder
4. IC 7474 – D Flipflop
5. IC 74x194 – 4 bit bidirectional universal shift register
6. IC 7483 - 4 bit parallel Adder
7. 555 Timer
8. Common Anode 7 segment Display
9. Resistors, Capacitors
10. Bread Board
11. DC power supply
12. Oscilloscope

Pin Diagram of Basic ICs


1. 555 Timer

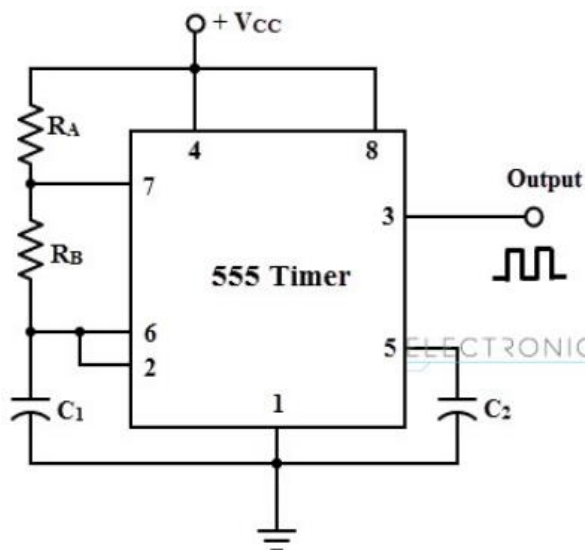


2. IC 7400 2-input NAND Gate

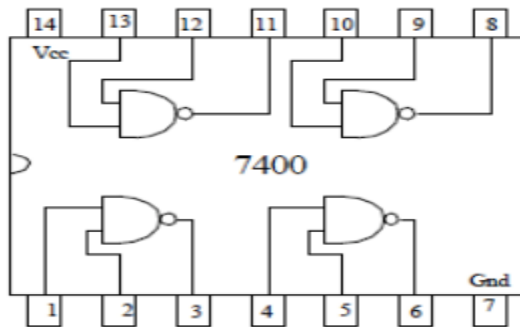


3. IC 7486 2-input XOR Gate

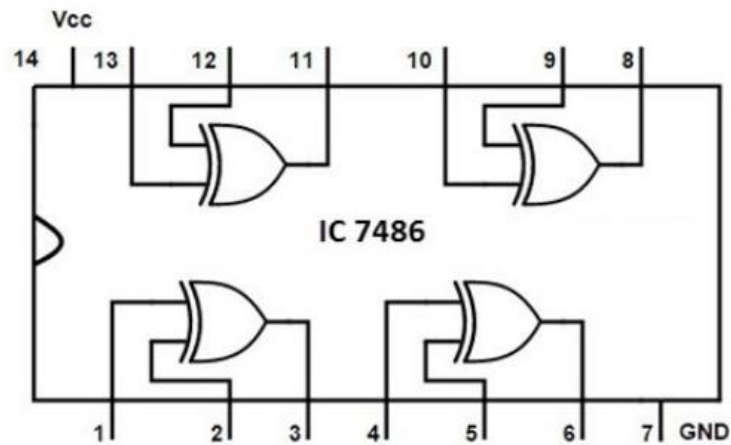


4. IC 7447 Decoder

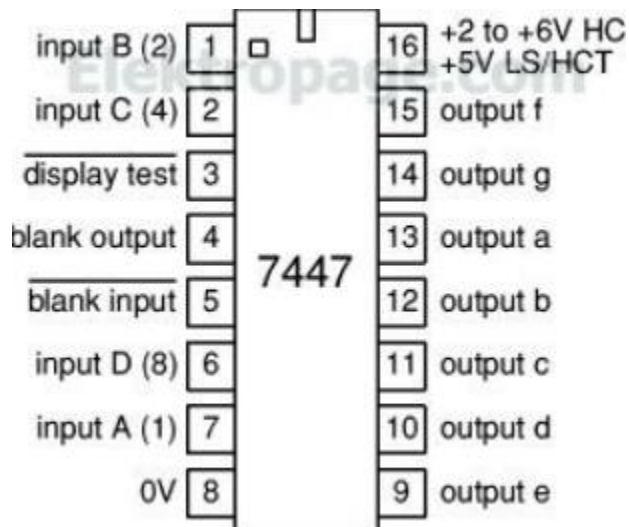


4. IC 7474 – D Flipflop

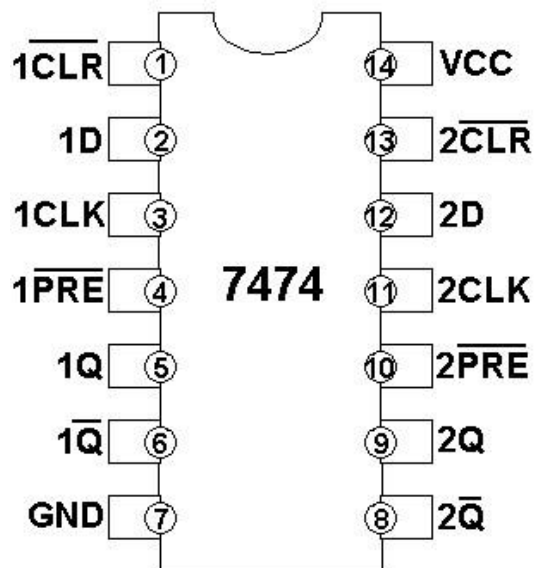


5. IC 74x194 – Shift Register

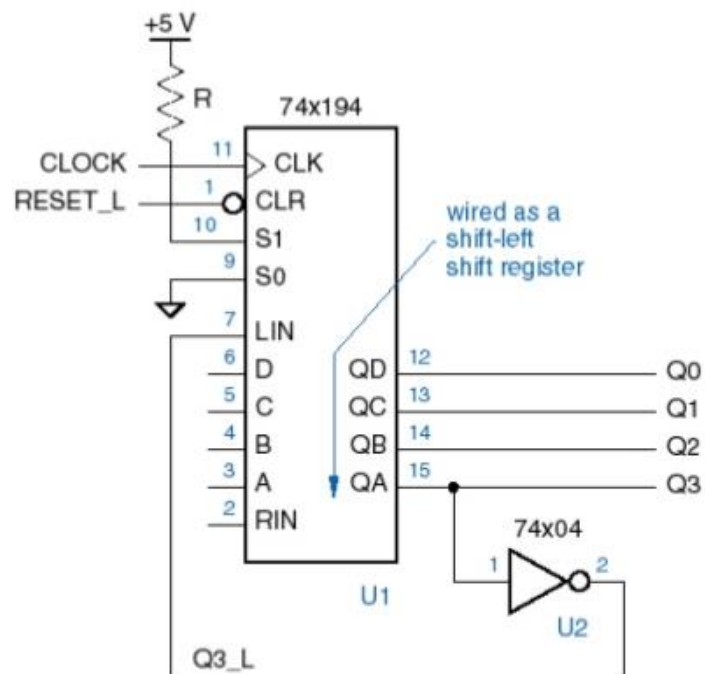

6. IC 7483 – 4 bit Adder

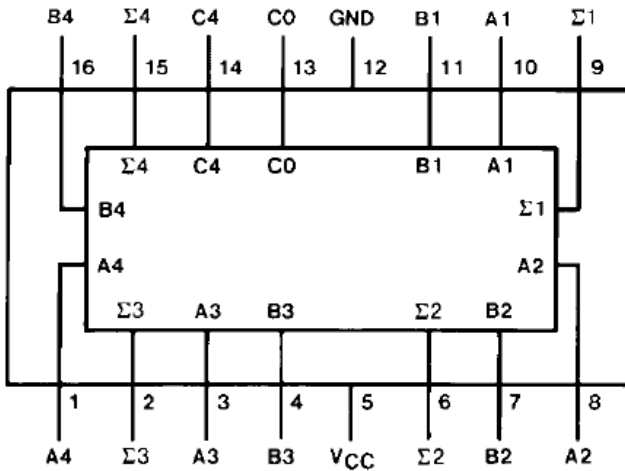

Circuit Diagram

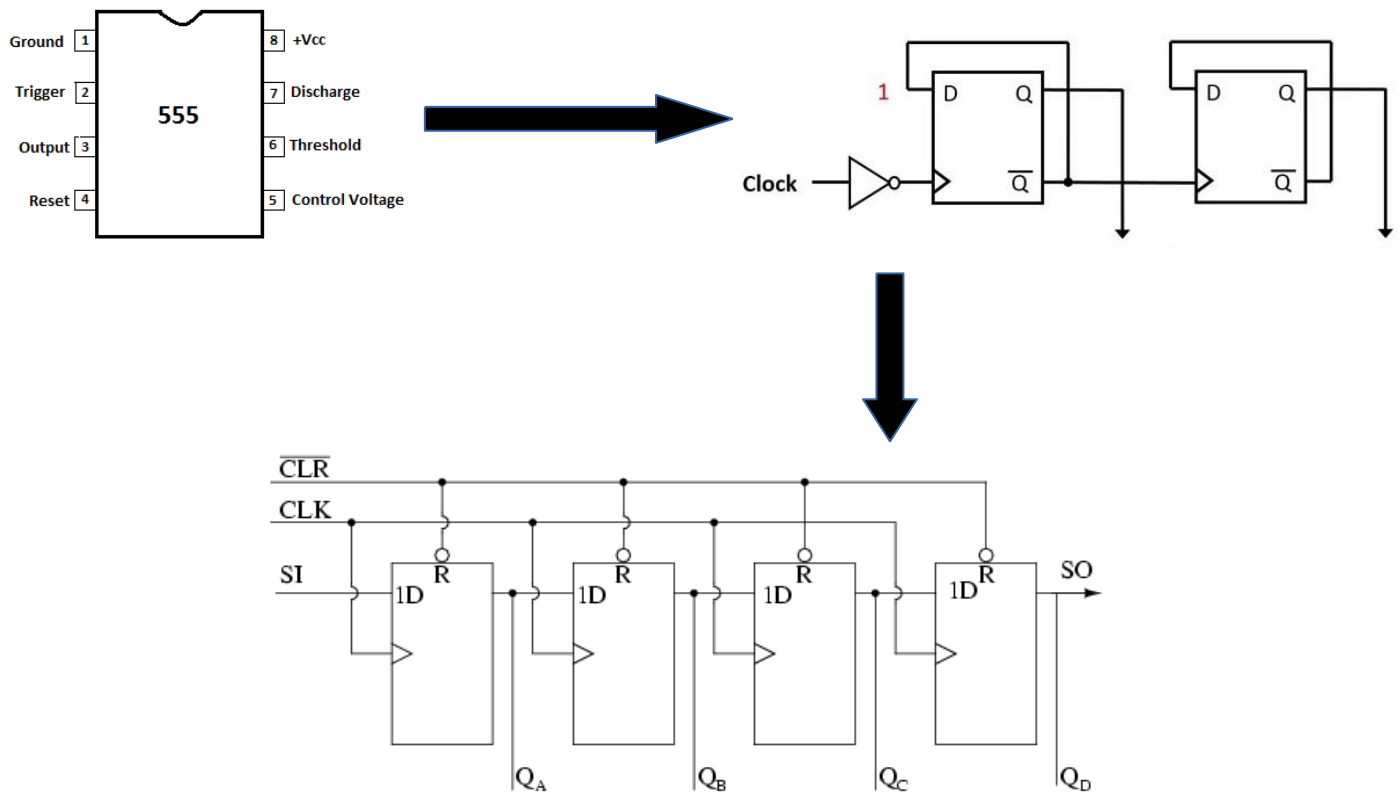

Serial-in/ Parallel out shift register details

