




# ECE380 Digital Logic

Implementation Technology:  
NMOS and PMOS Transistors,  
CMOS logic gates


 
## Logic values as voltage levels

- $V_{ss}$  is the minimum voltage that can exist in the system. We will use  $V_{ss}=0V$ .
- $V_{DD}$  is the power supply voltage. We will use  $V_{DD} = +5V$ .  $V_{DD} = +3.3V$  is also common.
- Exact levels of  $V_{0,max}$  and  $V_{1,min}$  depend on the implementation technology





## Transistor switches

- Logic circuits are built with transistors
- We will assume a transistor operates as a simple switch controlled by a logic signal  $x$
- The most popular type of transistor for implementing a simple switch is the **metal oxide semiconductor field effect transistor** (MOSFET)
- Two types of MOSFETs
  - N-channel (**NMOS**)
  - P-channel (**PMOS**)
- Early circuits relied on NMOS or PMOS transistors, but not both
- Current circuits use both NMOS and PMOS transistors in a configuration called **complementary MOS** (CMOS)


Electrical & Computer Engineering

Dr. D. J. Jackson Lecture 13-3



## NMOS transistor as a switch


$x = \text{"low"}$

 


$x = \text{"high"}$



 A simple switch controlled by the input  $x$



NMOS transistor

 



Simplified NMOS symbol

Electrical & Computer Engineering

Dr. D. J. Jackson Lecture 13-4



## NMOS transistor as a switch

  



- The transistor operates by controlling the voltage  $V_G$  at the gate terminal
- If  $V_G$  is low, there is no connection between the source and the drain terminals. The transistor is **turned off**.
- If  $V_G$  is high, the transistor is **turned on** and acts as a closed switch between the source and drain terminals.


  
## PMOS transistor as a switch





A simple switch controlled by the input x






## PMOS transistor as a switch

  

- The transistor operates by controlling the voltage  $V_G$  at the gate terminal
- If  $V_G$  is high, there is no connection between the source and the drain terminals. The transistor is **turned off**.
- If  $V_G$  is low, the transistor is **turned on** and acts as a closed switch between the source and drain terminals.



## NMOS and PMOS in logic circuits

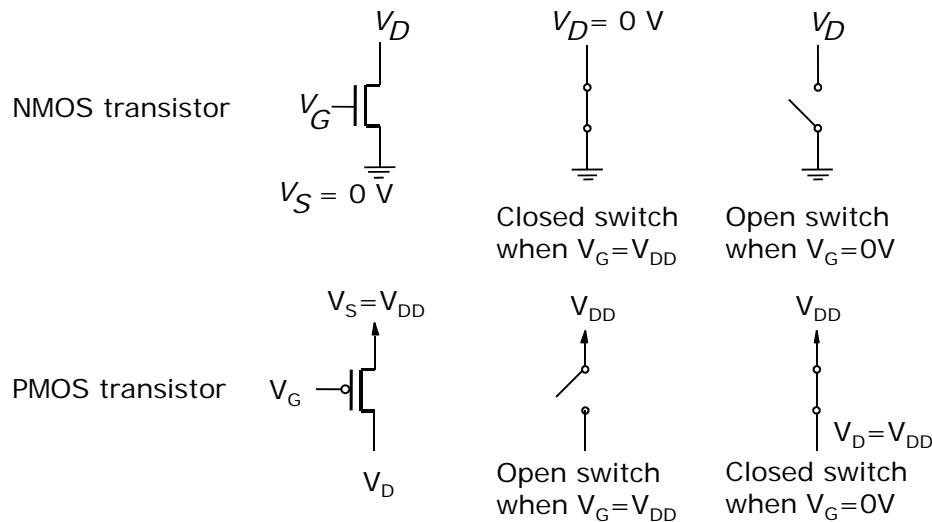



## NMOS and PMOS in logic circuits

---

- When the NMOS transistor is turned on, its drain is ***pulled down to Gnd***
- When the PMOS transistor is turned on, its drain is ***pulled up to  $V_{DD}$***
- Because of the way transistors operate:
  - An NMOS transistor cannot be used to pull its drain terminal completely up to  $V_{DD}$
  - A PMOS transistor cannot be used to pull its drain terminal completely down to Gnd
- Therefore, NMOS and PMOS transistors are commonly used in pairs in CMOS circuits



## CMOS logic gates


---

- A CMOS logic gate involves NMOS transistors in a ***pull-down network*** (PDN) and PMOS transistors in a ***pull-up network*** (PUN)
- The functions realized by the PDN and PUN networks are complements of one another
- The PDN and PUN have equal numbers of transistors, which are arranged so that the two networks are duals of one another
  - Wherever the PDN has NMOS transistors in series, the PUN has PMOS transistors in parallel, and vice versa


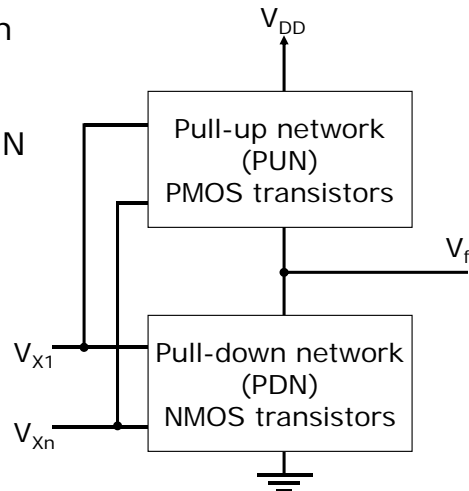
## CMOS logic gates

- For any given valuation of the input signals, either the PDN pulls  $V_f$  down to Gnd or the PUN pulls  $V_f$  up to  $V_{DD}$




Electrical & Computer Engineering


Dr. D. J. Jackson Lecture 13-11



## CMOS NOT gate

 

x	T1	T2	f
0	On	Off	1
1	Off	On	0

 


2 transistors

Electrical & Computer Engineering

Dr. D. J. Jackson Lecture 13-12



## CMOS NAND gate

 

X1	X2	T1	T2	T3	T4	f
0	0	On	On	Off	Off	1
0	1	On	Off	Off	On	1
1	0	Off	On	On	Off	1
1	1	Off	Off	On	On	0


4 transistors

Electrical & Computer Engineering

Dr. D. J. Jackson Lecture 13-13



## CMOS NOR gate

 

X1	X2	T1	T2	T3	T4	f
0	0	On	On	Off	Off	1
0	1	On	Off	Off	On	0
1	0	Off	On	On	Off	0
1	1	Off	Off	On	On	0


4 transistors

Electrical & Computer Engineering

Dr. D. J. Jackson Lecture 13-14




## CMOS AND gate

 

6 transistors



## CMOS OR gate

 


6 transistors






## CMOS non-inverting buffer

 

A non-inverting buffer

 



4 transistors

Electrical & Computer Engineering

Dr. D. J. Jackson Lecture 13-17



## CMOS transmission gate

  

$s$	$f$
0	Z
1	x


2 transistors

Electrical & Computer Engineering


Dr. D. J. Jackson Lecture 13-18



## CMOS tri-state buffer

 

<i>e</i>	<i>x</i>	<i>f</i>
0	0	Z
0	1	Z
1	0	0
1	1	1

 

8 transistors