

29/10/2019

Magnetic Circuits


- 1) Sinusoidal Analysis
- 2) AC & DC power
- 3) Magnetic Coupling \rightarrow self inductance & mutual inductance
- 4) Transformers
- 5) Resonance

Resistor \rightarrow active (dissipates energy)

~~active~~

Inductor (L) \leftarrow passive
Capacitor \leftarrow store energy element

Q

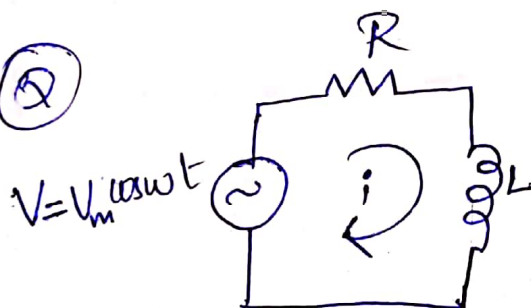

$$V_m \cos \omega t = Ri + L \frac{di}{dt}$$

$$I = I_1 \cos \omega t + I_2 \sin \omega t$$

$$V_m \cos \omega t = R(I_1 \cos \omega t) + R(I_2 \sin \omega t) + L(I_1)(-\sin \omega t)(\omega) + L(I_2)(\cos \omega t)(\omega)$$

$$\Rightarrow V_m \cos \omega t = [RI_1 + L I_2(\omega)] \cos \omega t + [RI_2 - L I_1(\omega)] \sin \omega t$$

$$I_1 = \frac{RV_m}{R^2 + \omega^2 L^2}$$

$$I_2 = \frac{\omega L(V_m)}{R^2 + \omega^2 L^2}$$

$$i(t) = \frac{RV_m}{R^2 + \omega^2 L^2} \overset{\cos 0}{\cos \omega t} + \frac{\omega L(V_m)}{R^2 + \omega^2 L^2} \overset{\sin 0}{\sin \omega t}$$

$$v(t) = V_m \cos \omega t$$

$$i(t) = I_m \cos(\omega t - \theta)$$

$$I_m = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \quad \theta = \tan^{-1}\left(\frac{\omega L}{R}\right)$$

Associativity + Homogeneity \rightarrow linearity

$$v_1(t) + j v_2(t) \rightarrow i_1(t) + j i_2(t)$$

$$V_m [\cos(\omega t + \theta) + j \sin(\omega t + \theta)] \rightarrow$$

$$I_m [\cos(\omega t + \phi) + j \sin(\omega t + \phi)]$$

$$V_m e^{j(\omega t + \theta)} \rightarrow I_m e^{j(\omega t + \phi)}$$

$$V_m e^{j\omega t} \cdot e^{j\theta} \rightarrow I_m e^{j\omega t} \cdot e^{j\phi}$$

$$\text{Re} [V_m e^{j\theta}] \rightarrow \text{Re} [I_m e^{j\phi}]$$

$$\rightarrow v(t) = V_m \cos \omega t \rightarrow \vec{V} = V_m \angle 0^\circ \rightarrow V_m \cos \omega t = \text{Re} [V_m \angle 0^\circ]$$

$$v(t) = R i(t)$$

$$i(t) = \frac{V_m}{R} \cos \omega t \quad \vec{I} = I_m \angle 0^\circ$$

$$\frac{v(t)}{i(t)} = R$$

\rightarrow Impedance - Restriction

\rightarrow equivalent impedance of Resistor is Z

(2) $i(t) = I_m \cos \omega t$

$$v(t) = L \frac{d(i(t))}{dt}$$

$$= L (I_m e^{j\omega t} j\omega)$$

$$= L j\omega (\vec{I})$$


$$\vec{V} = j\omega L \vec{I}$$

$$Z = \frac{\vec{V}}{\vec{I}} = j\omega L$$


$$\vec{I} = I_m \angle 0^\circ$$

$$= I_m e^{j\omega t}$$
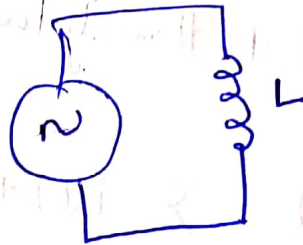
$$\frac{di}{dt} = I_m e^{j\omega t} (j\omega)$$



(3)

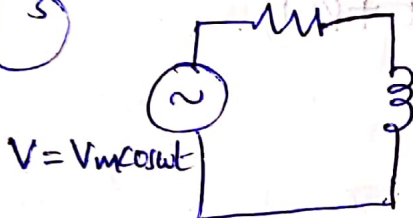

$$\vec{V} = V \angle 0$$


$$= \text{Re} [V e^{j\omega t}]$$

$$= V_m \cos \omega t$$

$$\vec{I} = \frac{\vec{V}}{R + j\omega L}$$

$$\vec{I} = \frac{V_m \angle 0}{Z_m \angle \phi}$$
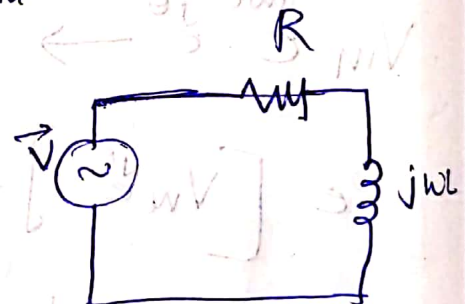
$$\vec{I} = \frac{V_m}{Z_m} \angle 0 - \phi$$



11/11/19

1) phasor notation

2) concept of lead & lag

3) concept of impedance

4) Re-collection of theorems - Thevenin & Norton

$V(t) = V_m \cos \omega t$ any circuit having L & C

→ Differential equations $\xleftrightarrow{\text{Transform}}$ linear set of equation

$$V(t) = V_m \cos \omega t + j V_m \sin \omega t$$

$$= V_m e^{j\omega t}$$

Time Domain

Phasor Domain

$$V_m \cos \omega t \rightarrow \text{Re} [V_m e^{j\omega t}] \rightarrow V_m \angle 0^\circ$$

$$V_m \cos(\omega t + \phi) \rightarrow \text{Re} [V_m e^{j(\omega t + \phi)}] \rightarrow V_m \angle \phi$$

$$V_m \sin \omega t \rightarrow$$

$$V_m \angle -90^\circ \rightarrow V_m \cos(\omega t - 90^\circ)$$

$$V_m \sin(\omega t + \phi) \rightarrow$$


$$V_m \angle \phi - 90^\circ$$

→ $\sin \omega t$ is lagging $\cos \omega t$ by $\pi/2$

$$\vec{V} \angle \theta = V_m \cos(\omega t + \theta)$$

$$\text{---} \underline{\underline{R}} \text{---} \quad I = \frac{V_m}{R} \cos(\omega t + \theta)$$
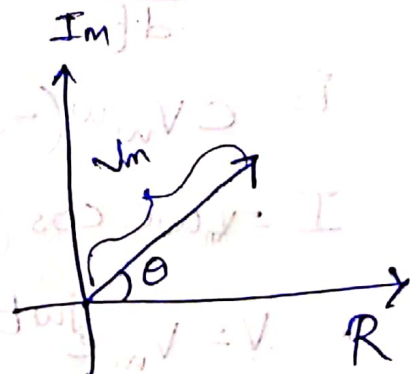
$$= \frac{\vec{V} \angle \theta}{R} = \vec{I}_m \angle \theta$$



$$V = L \frac{di}{dt} \rightarrow \text{cause}$$

effect

$$I_m \angle 0^\circ = I_m \cos \omega t$$

$$V = L \frac{d I_m \cos \omega t}{dt} = L(\omega) I_m (-\sin \omega t)$$

$$= I_m(\omega L) \cos(\omega t + 90^\circ)$$

$$\vec{V} = j\omega L (\vec{I})$$

$$I_m \cos \omega t \rightarrow \omega L I_m \cos(\omega t + 90^\circ)$$

$$\vec{V} = L \frac{di}{dt} = L \left(\frac{d I_m e^{j\omega t}}{dt} \right)$$

$$= L(\omega) j I_m e^{j\omega t}$$

$$V = L \frac{di}{dt} \Rightarrow I = I_m e^{j\omega t}$$

In pure Inductor

~~$$I = I_m \cos \omega t \angle 0^\circ$$~~


~~$$V = \omega L I_m \sin \omega t$$~~

$$V = L I_m (j\omega) e^{j\omega t}$$

$$= j\omega L \cdot (I_m e^{j\omega t})$$

$$= j\omega L \cdot \vec{I}$$
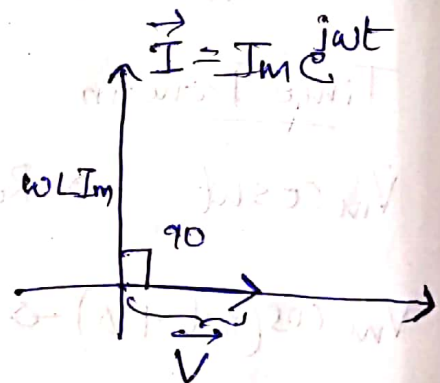
$$\vec{V} = (\omega L) \vec{I} \angle 90^\circ$$



voltage leads by 90°

For Capacitor

$$i = C \frac{dV}{dt}$$


$$V = V_m \cos \omega t$$

$$i = C V_m \omega (-\sin \omega t)$$

$$I = V_m \omega C \cos(\omega t + 90^\circ)$$

$$V = V_m e^{j\omega t}$$

$$\vec{I} = j\omega C \vec{V}$$

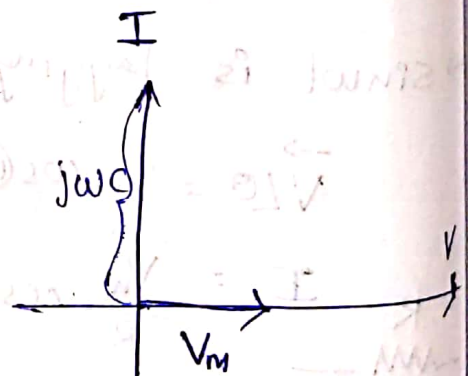

~~$$\vec{I} = \frac{I_m}{\omega L} \angle -90^\circ$$~~

$$\vec{V} = \frac{1}{j\omega C} \vec{I} = \frac{-j}{\omega C} \vec{I}$$

$$V = L \frac{dIm \cos \omega t}{dt} = -\omega L Im \sin \omega t$$

$$= \omega L Im \cos(\omega t + 90^\circ)$$


In Resistance - both V, I are in same phase
 In Capacitor - voltage lags current by 90°

Z - Impedance


$$\text{Reactance} = \frac{V}{I}$$

$$\vec{V} = \vec{Z} \vec{I} \quad \vec{I} = \frac{\vec{V}}{\vec{Z}}$$


	Z	Y
R	R	$1/R$
L	$j\omega L$	$-j/\omega L$
C	$\frac{-j}{\omega C}$	$j\omega C$

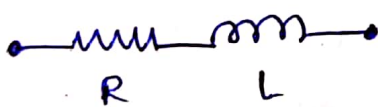

$$Z_1 = R + j\omega L$$

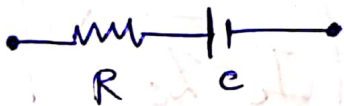


$$Z_2 = R - \frac{j}{\omega C}$$

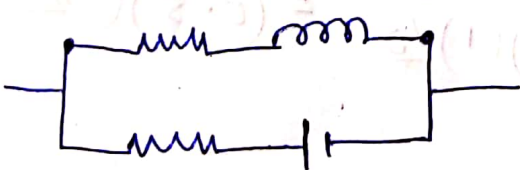

$$Z = \frac{Z_1 Z_2}{Z_1 + Z_2}$$

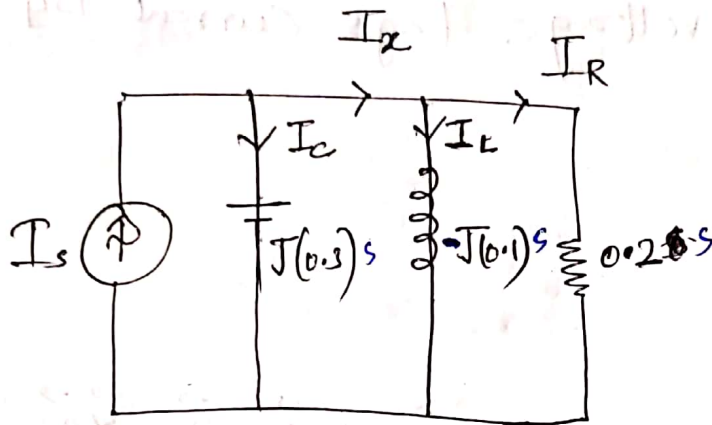① construct Phasor diagram showing I_R , I_L , I_C for the below circuit. Determine the angle by which I_S leads I_R , I_C and I_X .



$$V = I_m \cos \omega t$$

$$V = 1 \angle 0^\circ$$

$$\vec{V} = \vec{Z} \vec{I}$$

$$\Rightarrow I_S = I_X + I_C$$

$$\Rightarrow \vec{V} = \frac{1}{j\omega C} \vec{I}_C$$

$$\vec{V} = \omega L \vec{I}_L$$

$$\vec{V} = (0.2) \vec{I}_R$$

$$I_X = I_R + I_L$$

$$= \frac{\vec{V}}{0.2} + \frac{\vec{V}}{\omega L}$$

$$I_S = \frac{\vec{V}}{0.2} + \frac{\vec{V}}{\omega L} + j\omega C \vec{V}$$

so,

$$I_R = GV$$

$$= (0.2)(1) \angle 0^\circ$$

$$= 0.2 \angle 0^\circ$$

$$I_L = \frac{1}{Z_L} V$$

$$= (0.1)(1) \angle 0^\circ$$

$$I_C = \frac{1}{Z_C} (V)$$

$$= (0.3)(1) \angle 0^\circ$$

$$I_X = 0.2 + 0.1$$

$$= 0.3$$

$$I_S = I_X + I_C$$

$$= 0.3 + 0.3$$

$$= 0.6 \angle 0^\circ$$

$$= 0.6 \cos \omega t$$

$$\frac{\omega t - \pi/2}{\omega t} = 1 - \frac{\pi/2}{\omega t}$$

$$= 0.2 \angle 0^\circ + 0.1 \angle -90^\circ$$

$$= 0.2 \cos \omega t + 0.1 \sin \omega t$$

$$= \sqrt{(0.2)^2 + (0.1)^2} \left(\tan^{-1} \left(\frac{b}{a} \right) \right)$$

$$I_L = -j(0.1) \angle 0 = 0.1 \angle -90 = 0.1 \sin \omega t = 0.1 \angle -90 = 0.1 \cos(\omega t - 90)$$

$$I_C = j(0.3) \angle 0 = 0.3 \angle 90 = 0.3 \cos(\omega t + 90)$$


$$I_S = I_C + I_L = 0.2 + j0.2 = 0.283 \angle 45^\circ$$

$$I_X = 0.224 \angle -26.6^\circ = (0.2 \angle 0 + 0.1 \angle -90)$$

$$0.3 \cos(\omega t + 90)$$

$$= 0.3$$
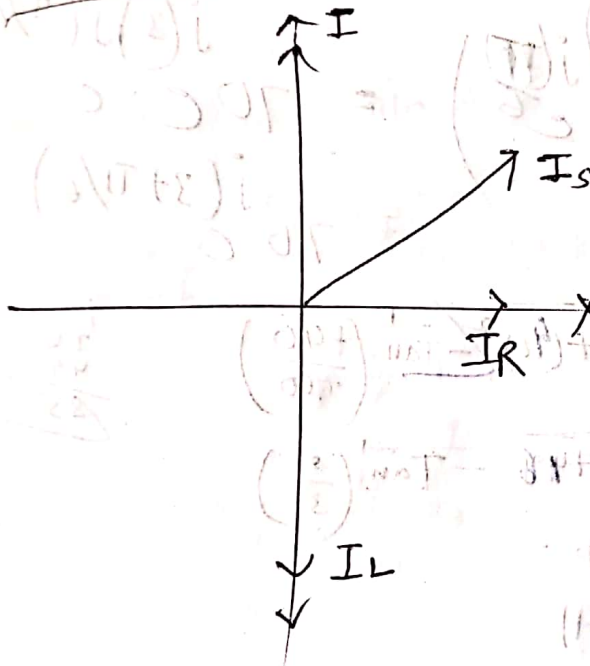
$$a - jb = \sqrt{a^2 + b^2} \angle -\tan^{-1} \left(\frac{b}{a} \right)$$




$$0.2 - j(0.1) =$$

$\Rightarrow I_S$ leads I_R by 45°

$\Rightarrow I_C$ by -45°

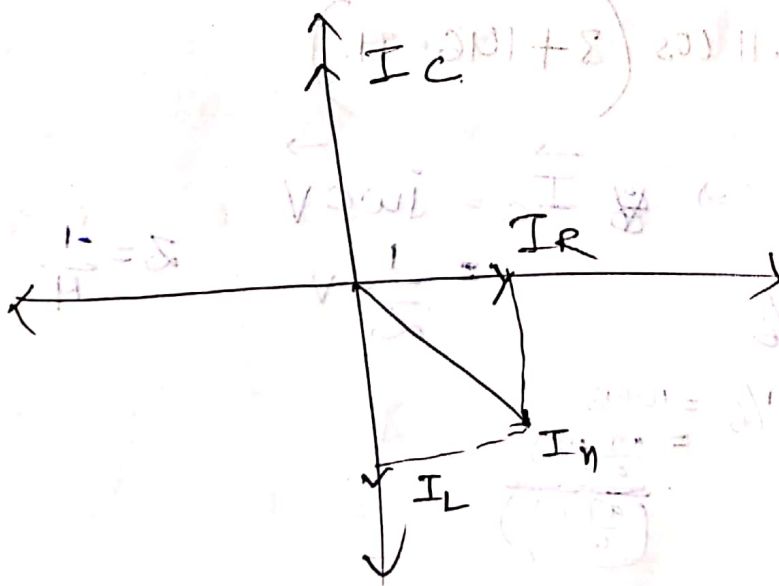$\Rightarrow I_X$ by $45 - (-26.6) = 71.6$



$$\vec{V} = \vec{I} \otimes \vec{I}_L = \frac{j}{\omega L} (\vec{V})$$

$$\vec{V} = j\omega L \vec{I}_L = \vec{I}$$

$$\vec{I}_C = j\omega C \vec{V}$$

Q If $\omega = 600 \text{ rad/s}$, $t = 5 \text{ msec}$ Find inst value

(a) $70 \angle 30^\circ$ (b) $-60 + 40j$

$$V(t) = V_m \cos \omega t = \text{Re}[V_m e^{j\omega t}]$$

$$= 70 \left[e^{j(6t + 30)} \right] = 70 \cos(\omega t + 30)$$

$$= 70 \left(e^{j(600 \times 5 \times 10^{-3})} e^{j(30)} \right) = 70 \cos\left(3 + \frac{\pi}{6}\right) = -64.95 \text{ V}$$

$$= 70 \left(e^{j(3)} e^{j(\pi/6)} \right) = 70 e^{j(3 + \pi/6)}$$

(b) $-60 + 40j = \sqrt{(-60)^2 + (40)^2} \angle -\tan^{-1}\left(\frac{+40}{+60}\right)$

$$\frac{36}{49} = \frac{85}{85}$$

$a - jb$

$a = -60$
 $b = -40$

$$= 10 \sqrt{36 + 16} \angle -\tan^{-1}\left(\frac{2}{3}\right)$$

$$= 12.1$$


(c) $V = 12.1 \cos(3 + 146.31)$

$$I_C = \frac{-j}{\omega C} \vec{V} \Rightarrow \vec{I}_C = j\omega C \vec{V}$$

$$= 2 + \frac{1}{4} = 8 + \frac{1}{6} = \frac{1}{Z} V \quad Z = \frac{1}{H}$$


$$= 8 + 8 + \frac{1}{6} = 16 + \frac{1}{6} = \frac{97}{6} \left(\frac{1}{3}\right) = \frac{97 + 1}{6}$$

Find I

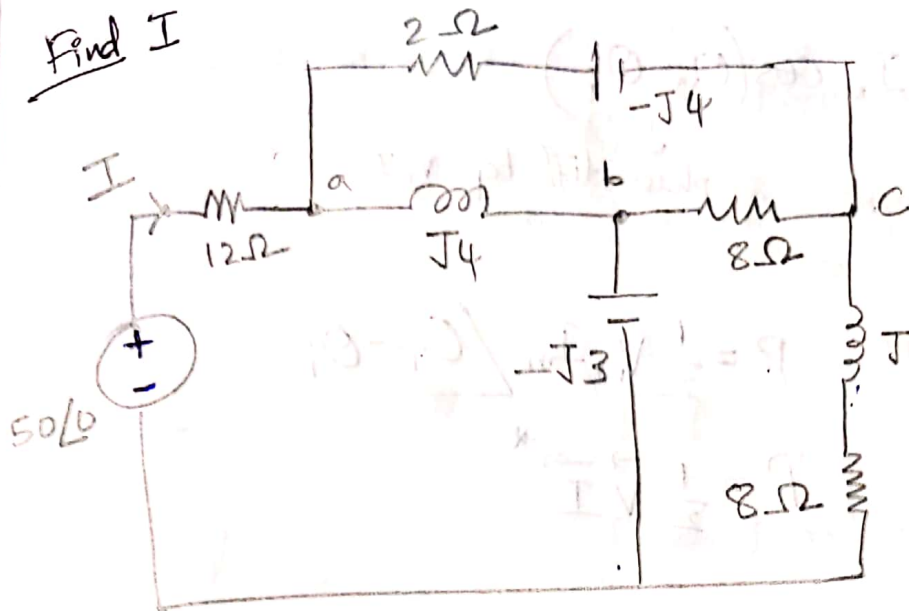

$$I = 3.66 \angle 4.2^\circ \text{ A}$$

Find V_x for following circuit

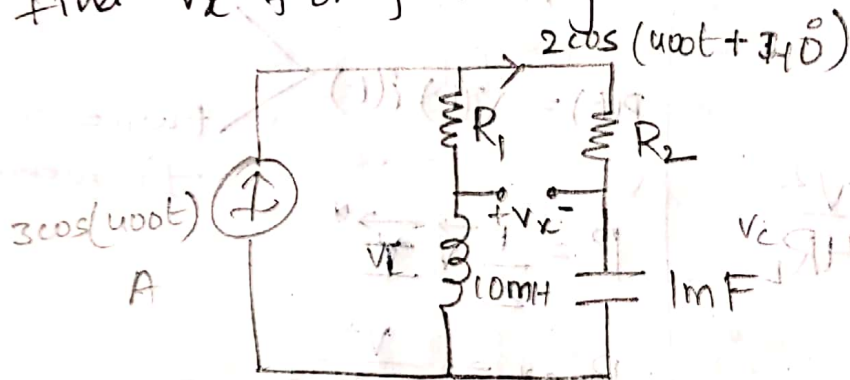

$$V_x = 9.892 \angle 78.76^\circ$$

6/11/19

observation time

$t \rightarrow \infty$ steady state

$$v(t) = V_m \cos(\omega t + \phi)$$

$$\vec{V} = V_m \angle \phi$$

$$\rightarrow P = I^2 R = I(V)$$

$$P(t) = I(t) \cdot V(t)$$

$$v(t) = V_m \cos(\omega t + \theta_v)$$

$$i(t) = I_m \cos(\omega t + \theta_i)$$

$$P(t) = \frac{1}{2} V_m I_m \left[\cos(\theta_v - \theta_i) \right] + \frac{1}{2} V_m I_m \cos(2\omega t + \theta_v + \theta_i)$$

$$P_{avg} = \frac{1}{T} \int_0^T P(t) dt \quad \text{the avg of cosine fun over its period} = 0$$

$$P_{avg} = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

↓
phase diff b/w V, I

$$\vec{V} = V_m \angle \theta_v$$

$$\vec{I} = I_m \angle \theta_i \quad P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

$$\vec{I}^* = I_m \angle -\theta_i \quad P = \frac{1}{2} \vec{V} \vec{I}^*$$

(complex conjugate)

DC	AC
$P = VI$ $P_{max} = \frac{V^2}{4R_L}$	$P(t) = v(t) i(t)$ $P = \frac{1}{2} \vec{V} \vec{I}^*$ $P_{max} = \frac{V^2}{8R_L}$

independent frequency
twice the frequency


$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

In Resistor $\theta_v = \theta_i$

$$P = \frac{1}{2} V_m I_m = \frac{1}{2} I_m^2 R \quad \text{more power dissipated}$$

In pure inductor (or) capacitor $P = 0$

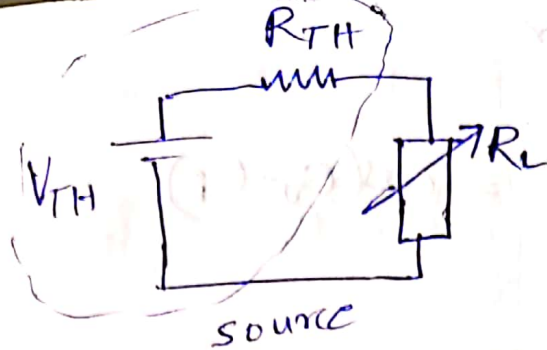→ using sinusoidal analysis we can convert it into any arbitrary signal.




$$R_{TH} = R_L$$

Thevenin Resistance = loaded Resistance

$$I = \frac{V_{TH}}{R_L + R_{TH}}$$

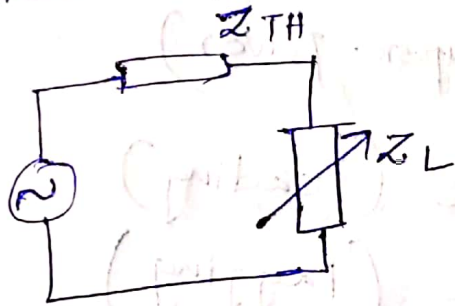→ maximum power transfers when $Z_{TH} = Z_L^*$



$$\frac{\partial P}{\partial R_L} = 0 \quad \frac{\partial P}{\partial X_L} = 0$$

$$P = I^2 R$$

$$P = \frac{1}{T} \int_0^T I^2 R dt = \frac{R}{T} \int_0^T I^2 dt = R \cdot I_{eff}^2$$

for any periodic function

$$I_{eff} = \sqrt{\frac{1}{T} \int_0^T i^2 dt} = I_{rms}$$

$$i = I_m \cos \omega t$$

$$I_{rms} = \frac{I_m}{\sqrt{2}}$$

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

$$= \frac{1}{2} \frac{V_{rms}(\sqrt{2})}{\sqrt{2}} \frac{I_{rms}(\sqrt{2})}{\sqrt{2}} \cos(\theta_v - \theta_i) = V_{rms} I_{rms} \cos(\theta_v - \theta_i)$$

$$P = V_{rms} I_{rms} \cos(\theta_v - \theta_i) = S \cos(\theta_v - \theta_i)$$

$S \rightarrow$ Apparent power

$$\text{powerfactor } (P_f) = \frac{P}{S} = \cos(\theta_v - \theta_i)$$

$$\vec{S} = \vec{P} + j\vec{Q}$$

$$\vec{P} = S \cos(\theta_v - \theta_i); \vec{Q} = S \sin(\theta_v - \theta_i)$$


$$S \rightarrow \text{VA}$$

$$P \rightarrow \text{W}$$

$$Q \rightarrow \text{VAR (voltage-Ampere-power)}$$

$$\theta_v < \theta_i \quad Q \rightarrow -ve \text{ (leading)}$$
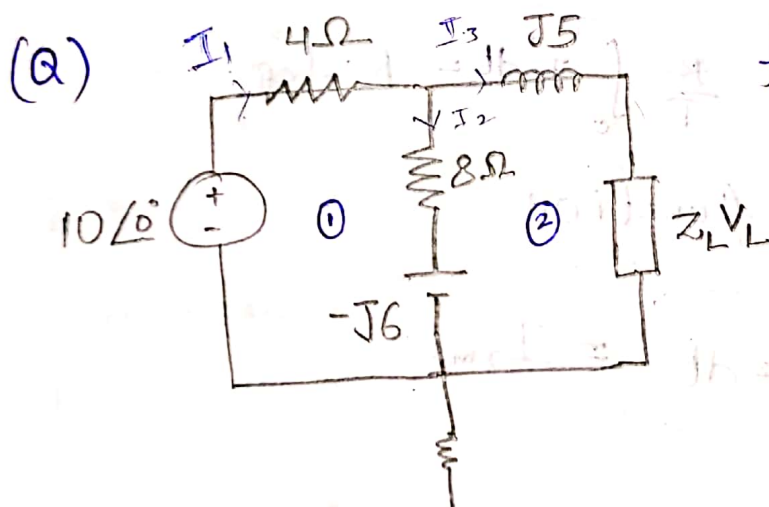
$$\theta_v > \theta_i \quad Q \rightarrow +ve \text{ (lagging)}$$



find P_{\max} delivered to ' Z_L '

$$P_{\max} = \frac{V_L^2}{8R_L}$$

$$\Rightarrow \vec{V} = j\omega L \vec{I}$$

$$\vec{V} = Z_L \vec{I}$$

$$\vec{V} \Rightarrow 10\angle 0^\circ = 5\vec{I}_L$$

$$\vec{V}_L$$

$$\vec{V} = \vec{I}_3 (5 + Z_L)$$

$$\vec{I}_3 = \frac{\vec{V}}{5 + Z_L}$$

$$\vec{V} = \vec{I}_2 (8 - j6)$$

loop 1:

$$\rightarrow 10\angle 0^\circ - (I_1(4) + I_2(8) + I_2(-j6)) = 0$$

loop 2:

$$I_3(j5) + (-I_2 8) - I_2(-j6) + Z_L(I_3) = 0$$



loop 3:

$$I_1(4) + I_3(j5) + Z_L(I_3) - 10\angle 0^\circ = 0$$

$$\rightarrow 10\cos\omega t - 4I_1 - 8I_2 + I_2(j6) = 0$$

$$\Rightarrow 10\cos\omega t - 4I_1 + I_2(6j - 8) = 0$$

$$5jI_3 - 8I_2 + 6jI_2 + Z_L I_3 = 0$$

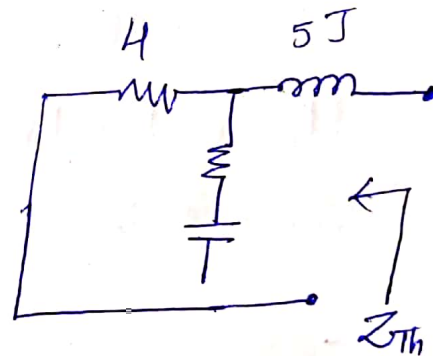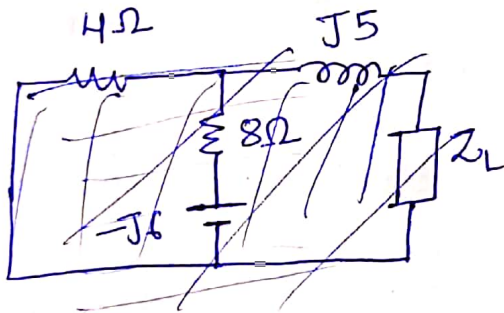

$$Z_{TH} = j5 + 4 \parallel (8 - j6)$$

$$P_{max} = \frac{V_{Th}^2}{8 R_L}$$


$$Z_L = Z_s^* = Z_{Th}^* = (R_L - jX_L)$$

$$V_{Th} = 10 \left(\frac{8 - j6}{8 - j6 + 4} \right)$$

$$V_L = 7.454 \angle -10.3^\circ$$

$$Z_L = 2.933 - j4.467 \Omega$$

$$P_{max} = 2.368 W$$

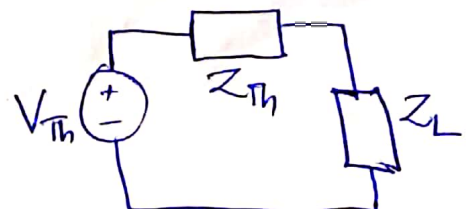

$$8 - j6 = \sqrt{8^2 + 6^2} \angle -\tan^{-1}\left(\frac{6}{8}\right)$$

$$= 10 \angle -\tan^{-1}(3/4) = 10 \angle -36.8^\circ$$

① complex power (S) = $P + jQ = V_{rms} \cdot I_{rms}^*$

② Apparent power (S) = $V_{rms} \cdot I_{rms} = |S|$


③ Real power (P) = $\text{Re}(S)$ (magnitude)

④ Reactive Power (Q) = $\text{Im}(S)$

⑤ power factor = $P/S = \cos(\theta_v - \theta_i)$

$$Z_{TH} = 4 + (-j368.6) \neq 5j = 5j - 364.6$$

=

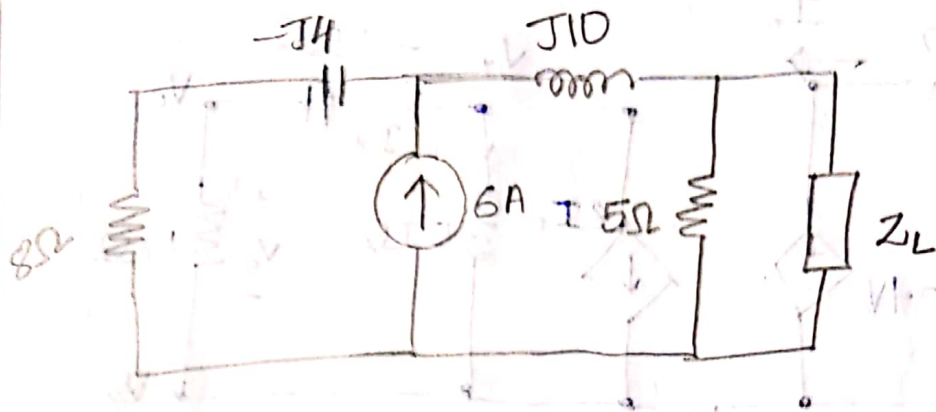

Find Z_L for
max. avg power
(P_{max})

② The voltage across a load is $V_t(\text{instantaneous}) = 60 \cos(\omega t - 10^\circ)$
and the current through element T in direction of the voltage drop is $i_t = 1.5 \cos(\omega t + 50^\circ)$. Find the complex and apparent power. The real and reactive power, power factor and load impedance.

(sd) \Rightarrow complex power (S) = $45 \angle -60^\circ$

\Rightarrow Apparent power $|S| = VI + (I^2)R$

$P(t) = V(t) \cdot I(t) = 60 \cos(\omega t - 10^\circ) \cdot 1.5 \cos(\omega t + 50^\circ)$

$P_{avg} = V_{rms} \cdot I_{rms} \cos(\theta_V - \theta_I)$

$= \frac{60}{\sqrt{2}} \cdot \frac{1.5}{\sqrt{2}} \cos(-10^\circ - 50^\circ)$


Real power = $\frac{60}{\sqrt{2}}$

$= \frac{60 \times 1.5}{2} \cos(-60^\circ)$

$= 45 \cos(-60^\circ)$

$\Rightarrow 22.5 \text{ W}$

(0.4)

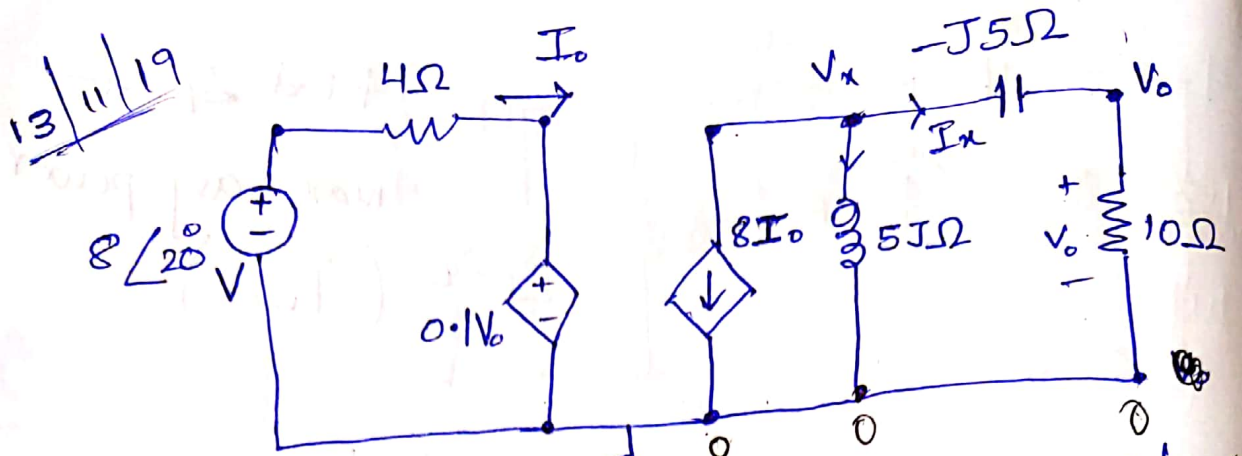

Find avg power absorbed by 10Ω resistor

$$P_{avg} = I(t) v(t) = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

$$\Rightarrow 10 - 5j \Rightarrow \sqrt{(10)^2 + (5)^2} \angle -\tan^{-1}\left(\frac{5}{10}\right)$$

$$\Rightarrow = \sqrt{125}$$

$$= 11.18 \angle$$

$$\Rightarrow 4(I_0) + 0.1V_0 - 8\angle 20^\circ = 0$$

$$\Rightarrow 4(I_0) + 0.1V_0 - 8\cos(\omega t + 20^\circ) = 0 \rightarrow (1)$$

$$\Rightarrow -$$

$$V = j\omega L(I)$$

$$8I_0 + \frac{V_x}{5j} + \frac{V_x}{10 - 5j} = 0 \rightarrow (2)$$

$$V_0 =$$


$$I_x = \frac{V_0}{10}$$

$$V_0 = V_x \left(\frac{10}{10 - 5j} \right)$$

$$V_0 = \frac{80\angle 20^\circ}{(1+j)}$$


$$P_{avg} = I_{rms}^2 R_L$$

$$160W = \frac{1}{2} |I_x|^2 R_L$$

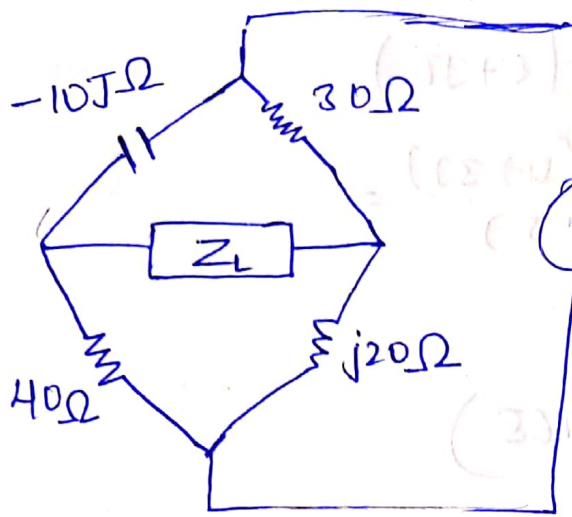

calculate $Z_L =$
max Avg power across Z_L

$Z_L \rightarrow$

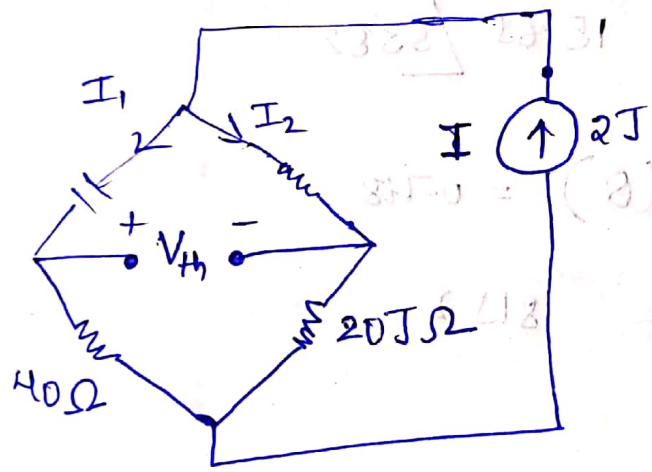


$$(Z_{Th})^* = (Z_L)^*, Z_L = Z_{Th}^* = 20 - j2$$

$$V_{Th} = 30I_2 + 10jI_1$$

$$I_2 = 2j \left(\frac{40 - 10j}{40 - 10j + 30 + 20j} \right)$$

$$I_1 = 2j \left(\frac{30 + 20j}{70 - 10j} \right)$$

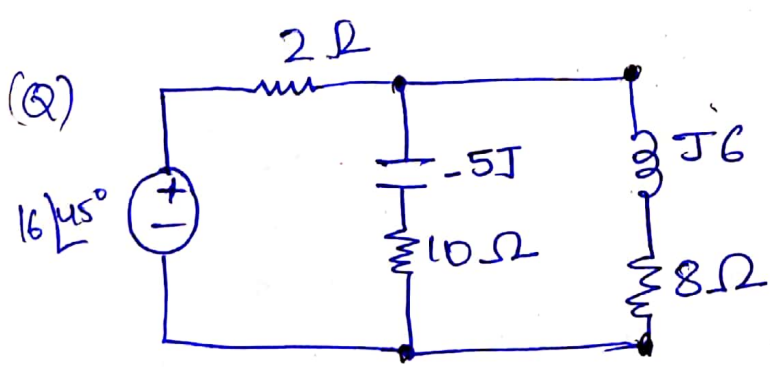\Rightarrow calculate Z_{Th} short circuit source, open circuit $2j\Omega$



$$a + bj$$

$$6j + 8$$

$$= \sqrt{36 + 64}$$

$$= 10 \tan^{-1} \left(\frac{6}{8} \right)$$

$$\Rightarrow \frac{(10 - 5j) \cdot (8 + 6j)}{(10 - 5j + 8 + 6j)} = \frac{(10 - 5j)(8 + 6j)}{(18 + j)} + 2$$

$$R =$$

$$\begin{aligned}
 Z_T &= 2 + (10 - j5) \parallel (8 + j6) \\
 &= 2 + \frac{10(2 - j)(4 + j3)}{(18 + j)} = \\
 &= 8.188 \angle 53.82^\circ \\
 &= 8.152 + j(0.768)
 \end{aligned}$$


$$PF = \cos(53.82) = 0.9956$$

$$avg = \frac{1}{2} \frac{|V|^2}{Z^*} = 15.63 \angle 53.82$$

$$Reactive\ power\ (Q) = 0.768$$

$$Real\ power = 8152$$

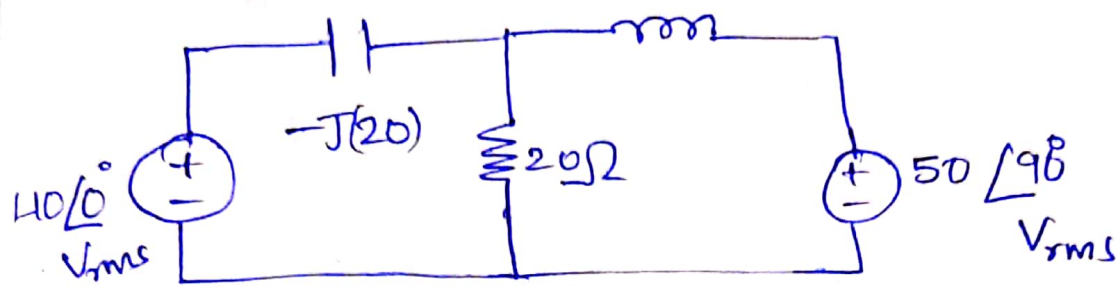(Q) find complex power absorbed by each element



$$\frac{60}{360}$$

→ Generator consist of stator (stationary) and rotor (motion)

→ 3-phase output

→ 3-phase voltage sources (a) Y-connected source
(b) Δ-connected

phase voltage - line voltage

phase current - line current