



ECE380 Digital Logic

Introduction to Logic Circuits:
Synthesis using AND, OR, and
NOT gates




Example logic circuit design

- Assume we want to design a logic circuit with three inputs x , y , and z
- The circuit output should be 1 only when $x=1$ and either y or z (or both) is 1
 - Three possible combinations
 - $x=1, y=0, z=1 \Rightarrow xy'z$
 - $x=1, y=1, z=0 \Rightarrow xyz'$
 - $x=1, y=1, z=1 \Rightarrow xyz$
- The function could be written as
 - $f(x,y,z) = xy'z + xyz' + xyz$
 - sum of products form



Example logic circuit design

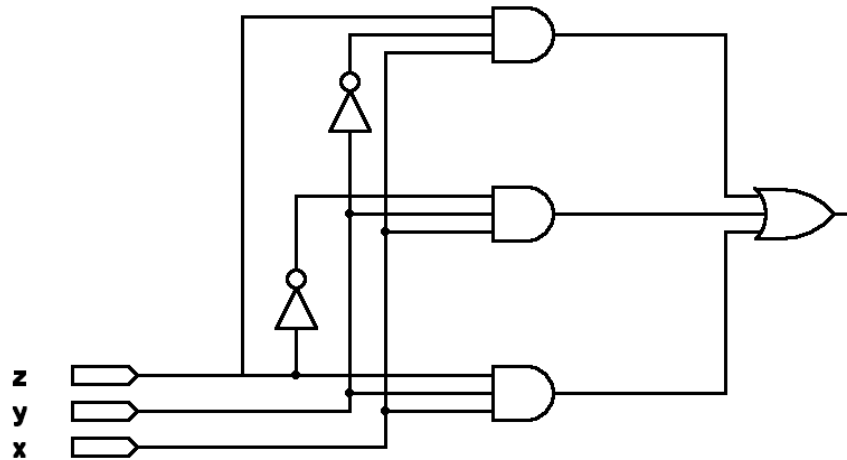

Electrical & Computer Engineering

Dr. D. J. Jackson Lecture 4-3



Example logic circuit design

- Implements f correctly, $f(x,y,z) = xy'z + xyz' + xyz$ but is not the simplest such network

| x | y | z | f |
|-----|-----|-----|-----|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 |

$$xy'z + xyz' + xyz$$

$$xy'z + xy$$


from 14a

$$x(y'z + y)$$

from 12a

$$x(y + z)$$

from 16a

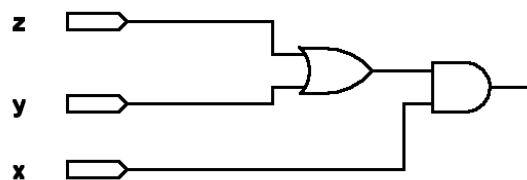

Electrical & Computer Engineering

Dr. D. J. Jackson Lecture 4-4



Example logic circuit design

- Obviously, the cost (in terms of gates and connections) of this network is much less than the initial network
- The process of generating a circuit from a stated desired functional behavior is called ***synthesis***
- Generation of AND-OR style networks from a truth table is one of many types of synthesis techniques that we will cover



Logic synthesis

- If a function f is described in a truth table, then an expression that generates f can be obtained (synthesized) by
 - Considering all rows in the table where $f=1$, or
 - By considering all rows in the table where $f=0$
- This will be an application of the principle of duality



Minterms

- For a function of n variables $f(a,b,c,...n)$
 - A minterm of f is a product of n literals (variables) in which each variable appears once in either true or complemented form, but not both
 - $f(a,b,c)$ -- minterm examples: abc , $a'bc$, abc'
 - $f(a,b,c)$ -- invalid examples: ab , c' , $a'c$
 - An n variable function has 2^n valid minterms



Minterms

| Row number | x | y | z | Minterm |
|------------|-----|-----|-----|----------------|
| 0 | 0 | 0 | 0 | $m_0 = x'y'z'$ |
| 1 | 0 | 0 | 1 | $m_1 = x'y'z$ |
| 2 | 0 | 1 | 0 | $m_2 = x'yz'$ |
| 3 | 0 | 1 | 1 | $m_3 = x'yz$ |
| 4 | 1 | 0 | 0 | $m_4 = xy'z'$ |
| 5 | 1 | 0 | 1 | $m_5 = xy'z$ |
| 6 | 1 | 1 | 0 | $m_6 = xyz'$ |
| 7 | 1 | 1 | 1 | $m_7 = xyz$ |

- Each row of a truth row corresponds to a single minterm
- When a function is written as a sum of minterms, the form is called a standard (or canonical) **sum-of-products**



Minterm notation

- An equation may be written in terms of m-notation

$$f(a,b,c) = m_0 + m_1 + m_2 + m_4$$

$$f(a,b,c) = a'b'c' + a'b'c + a'bc' + ab'c'$$

$$\begin{array}{cccc} \underbrace{000} & \underbrace{001} & \underbrace{010} & \underbrace{100} \\ 0 & 1 & 2 & 4 \end{array}$$

$$f(a,b,c) = \Sigma m(0,1,2,4)$$

| <i>a</i> | <i>b</i> | <i>c</i> | <i>f</i> |
|----------|----------|----------|----------|
| 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 0 |



Minterm notation examples

- What is the minterm notation for the following function?
– $f(a,b,c) = abc + a'bc + abc' + a'b'c$
- What is the function (in terms of variables) if the minterm notation is the following?
– $f(a,b,c) = \Sigma m(1,5,6,7)$



Logic synthesis

- Duality suggests that:
 - If it is possible to synthesize a function f by considering the truth table rows where $f=1$, then it should also be possible to synthesize f by considering the rows for which $f=0$.
- This approach uses the complement of minterms, which are called **maxterms**



Maxterms

| Row number | x | y | z | Maxterm |
|------------|-----|-----|-----|----------------------|
| 0 | 0 | 0 | 0 | $M_0 = x + y + z$ |
| 1 | 0 | 0 | 1 | $M_1 = x + y + z'$ |
| 2 | 0 | 1 | 0 | $M_2 = x + y' + z$ |
| 3 | 0 | 1 | 1 | $M_3 = x + y' + z'$ |
| 4 | 1 | 0 | 0 | $M_4 = x' + y + z$ |
| 5 | 1 | 0 | 1 | $M_5 = x' + y + z'$ |
| 6 | 1 | 1 | 0 | $M_6 = x' + y' + z$ |
| 7 | 1 | 1 | 1 | $M_7 = x' + y' + z'$ |

- Each row of a truth row corresponds to a single maxterm
- When a function is written as a product of maxterms, the form is called a standard (or canonical) **product-of-sums**



Maxterm notation

- An equation may be written in terms of M-notation

$$f(a,b,c) = M_3 \cdot M_5 \cdot M_6 \cdot M_7$$

$$f(a,b,c) = (a+b'+c')(a'+b+c')(a'+b'+c)(a'+b'+c')$$

$$\begin{array}{cccc} 0 & 1 & 1 & 1 & 0 & 1 & 1 & 1 \\ \underbrace{} & \underbrace{} & \underbrace{} & \underbrace{} & & & & \\ 3 & 5 & 6 & 7 & & & & \end{array}$$

$$f(a,b,c) = \Pi M(3,5,6,7)$$

| a | b | c | f |
|---|---|---|---|
| 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 0 |



Maxterm notation examples

- What is the maxterm notation for the following function?
– $f(a,b,c) = (a+b+c)(a'+b+c)(a+b+c')(a'+b'+c)$
- What is the function (in terms of variables) if the maxterm notation is the following?
– $f(a,b,c) = \Pi M(1,5,6,7)$




Sum-of-products and minimality

- A function expressed in standard sum-of-products (or product-of-sums) form may not be minimal

| <i>a</i> | <i>b</i> | <i>f</i> |
|----------|----------|----------|
| 0 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

$$f(a,b) = a'b' + a'b + ab = a' + b$$

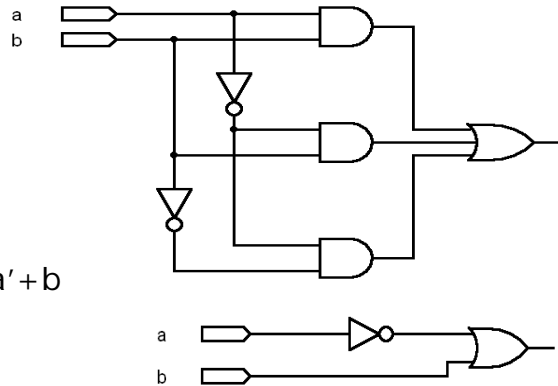

Electrical & Computer Engineering

Dr. D. J. Jackson Lecture 4-15



Form conversion

- If a function f is given in Σm or ΠM form, it is easy to find f or f' in Σm or ΠM form
- Use the following form conversion table

| GIVEN FORM | DESIRED FORM | | | |
|-----------------------------|---|---|---|---|
| | $f = \Sigma m$ | $f = \Pi M$ | $f' = \Sigma m$ | $f' = \Pi M$ |
| $f = \Sigma m$ (0,2,5,7) | -- | Use numbers <u>not</u> on minterm list (1,3,4,6) | Use numbers <u>not</u> on minterm list (1,3,4,6) | Use numbers on minterm list (0,2,5,7) |
| $f = \Pi M$ (1,3,4,6) | Use numbers <u>not</u> on maxterm list (0,2,5,7) | -- | Use numbers on maxterm list (1,3,4,6) | Use numbers <u>not</u> on maxterm list (0,2,5,7) |

Electrical & Computer Engineering

Dr. D. J. Jackson Lecture 4-16